
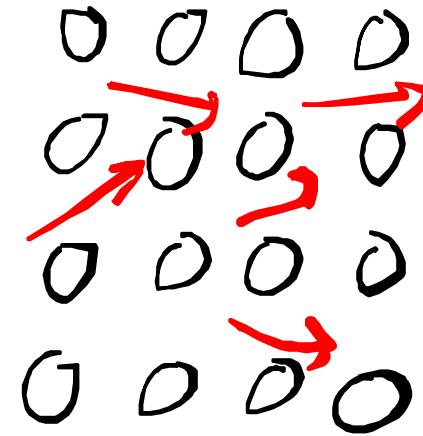



Atoms and Electrons

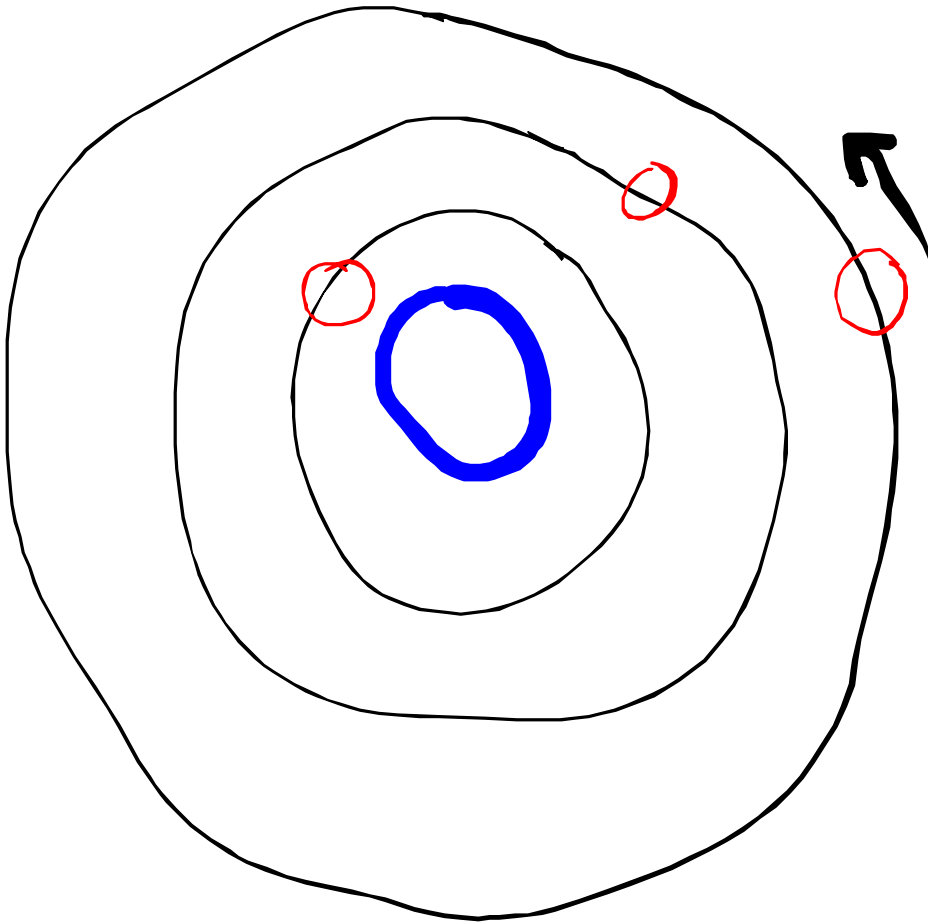

Electrons orbit the **nucleus**

Some electrons break free of the nucleus and can move freely through the metal.
Conduction electrons


Electric Circuits

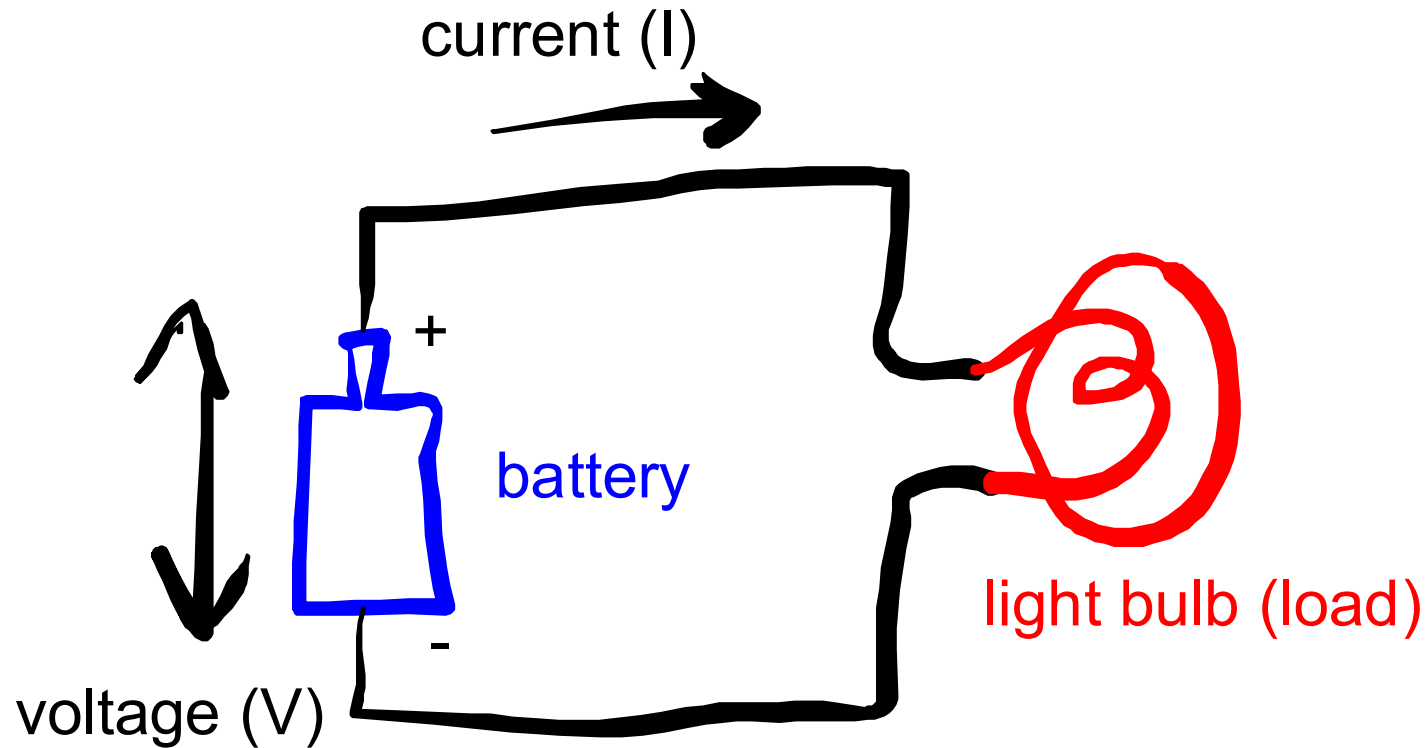

Current moves from + to -
(positive to negative)

Actually, electrons travel from - to +

Electric Circuits Resistance

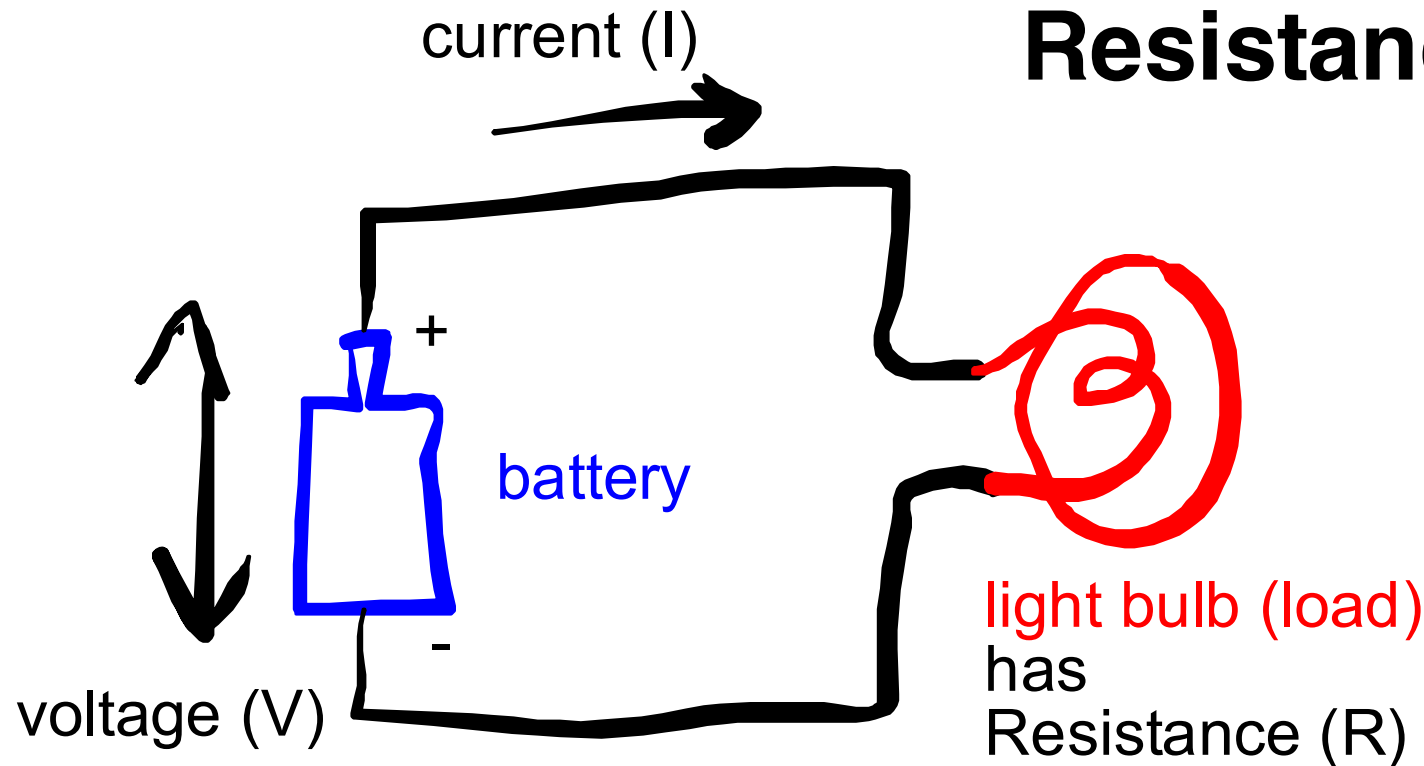

Ohm's Law: $V = I R$
voltage = current times resistance

If you have constant voltage:
small resistance gives big current
big resistance gives small current

Power

Power is energy released per time

Big power, lots of energy released per second

Small power, little energy released per second

$$P = V I$$

power = voltage times current

remember

$$V = I R$$

so

$$P = I R I$$

lower temperatures in materials mean less electron movement

which means less likely charges collide -> lower resistance

EXCEPT in semi-conductors. If no electrons are able to move, then resistance increases as well


$$P = I^2 R$$

power = current squared times resistance



Units of power are watts (W), 1 watt is 1 volt times 1 amp

Direct / Alternate Current


Current direction
is constant

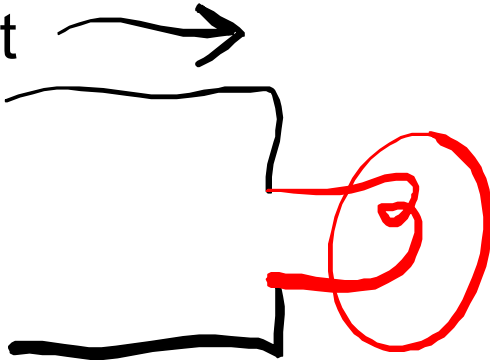

Current direction
changes

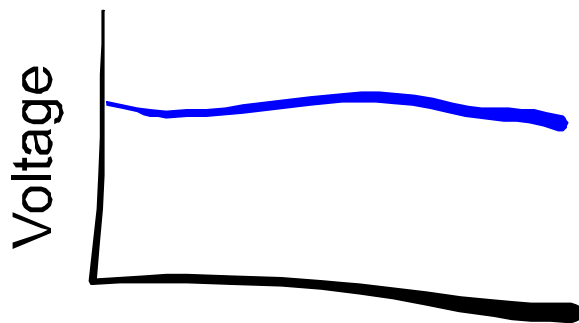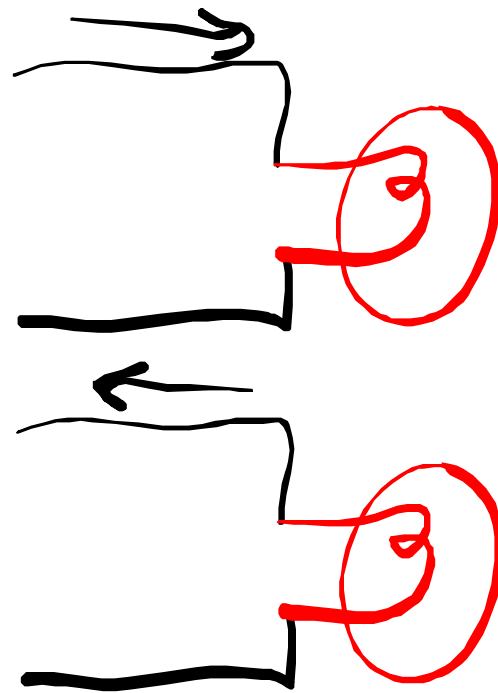


Voltage difference is
constant

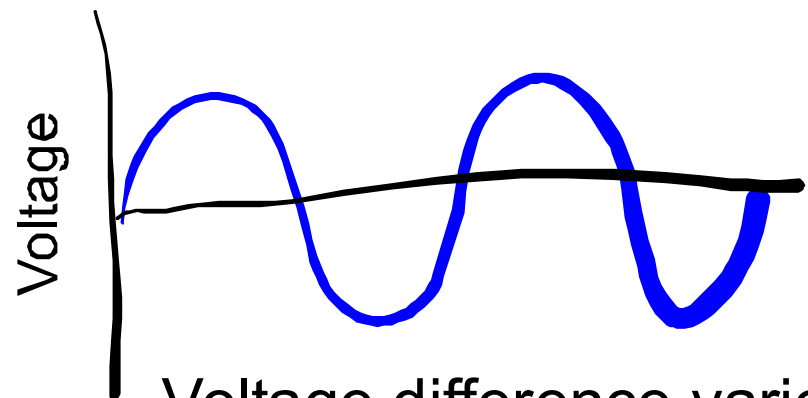

Voltage difference varies


Magnets

Magnetic field lines

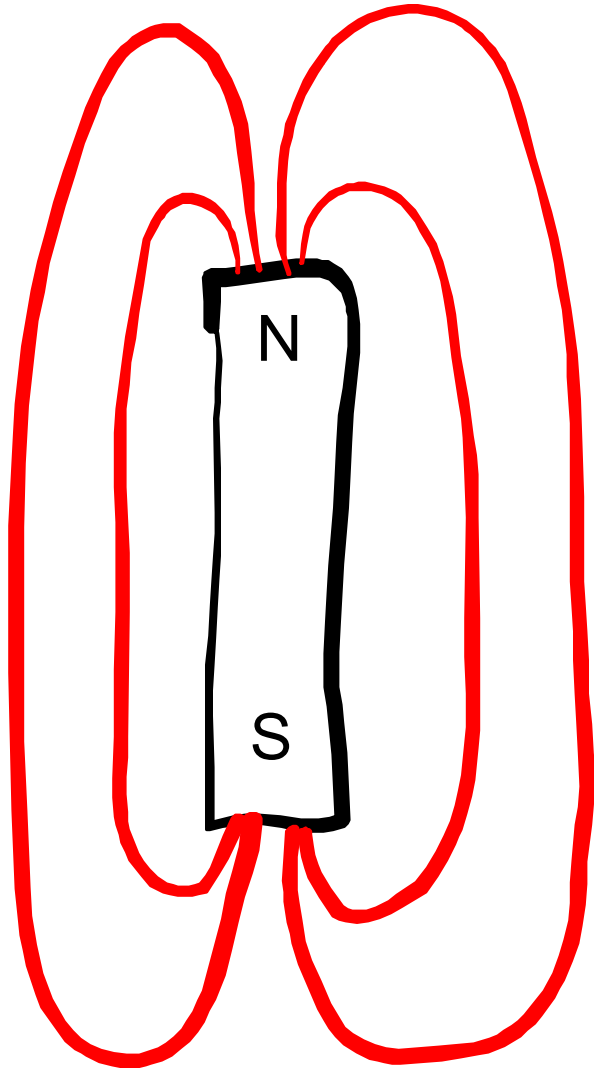

Permanent Magnet

Current in a coil


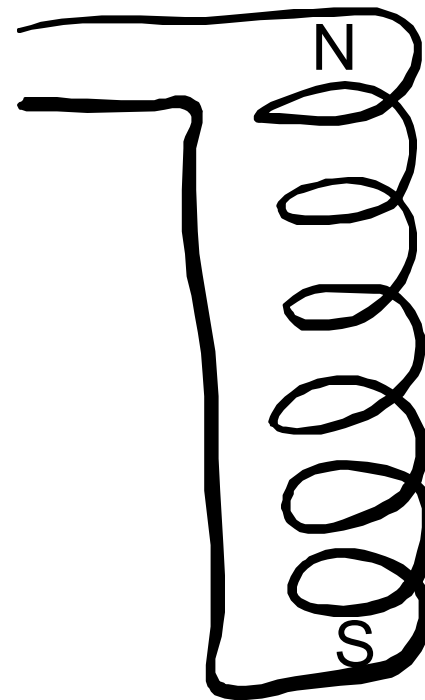


Electromagnet

Magnets and Electricity

Electric current makes a magnetic field

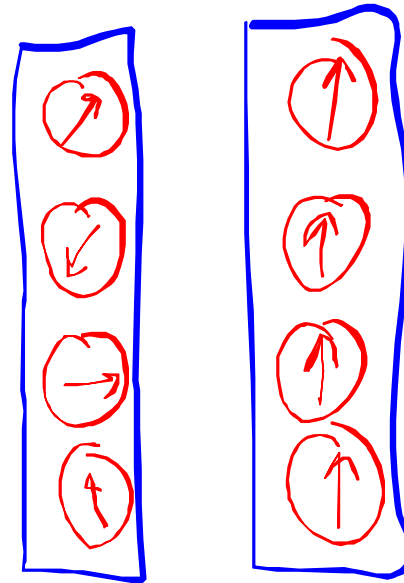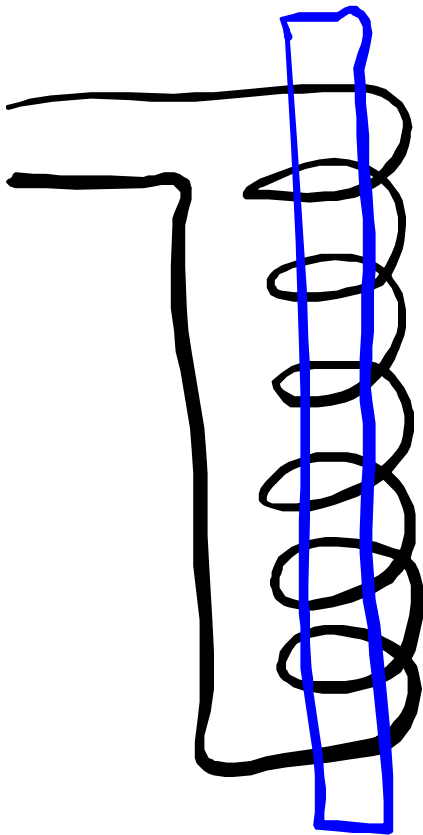Strength of field
depends on current
and number of windings




Iron bar has magnetic domains that are normally randomly oriented. They can be oriented by an external magnetic field.

This amplifies the total magnetic strength of the electromagnet

Magnets and Electricity

Changing magnetic field induces an electric field.

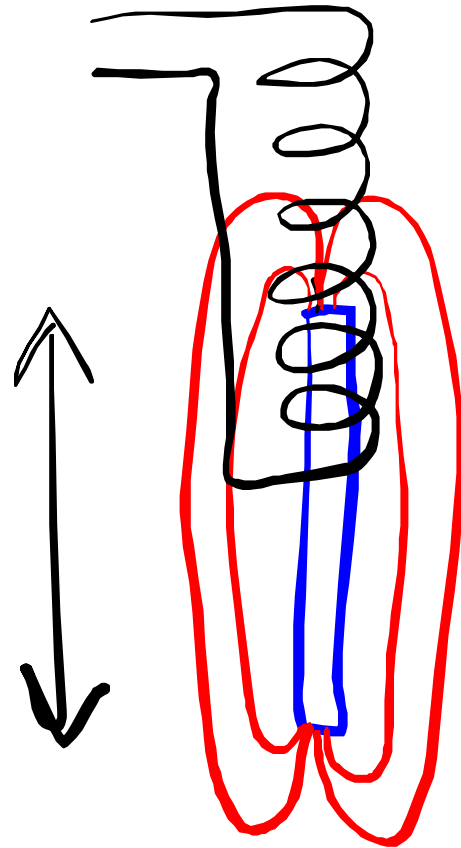Move permanent magnet in and out of coil to change magnetic field inside coil



Changing magnetic field inside coil induces voltage across the coil.
This voltage (and current) can power an electrical load (light bulb)

Lenz's Law


Lenz's Law: Current induced by a changing magnetic field always produces a magnetic field that opposes the change.

If I push the magnet into the coil, the coil will try to push back.


I need to do work on the magnet, this work gets transferred into electrical energy.

Use this to make a generator

Generator

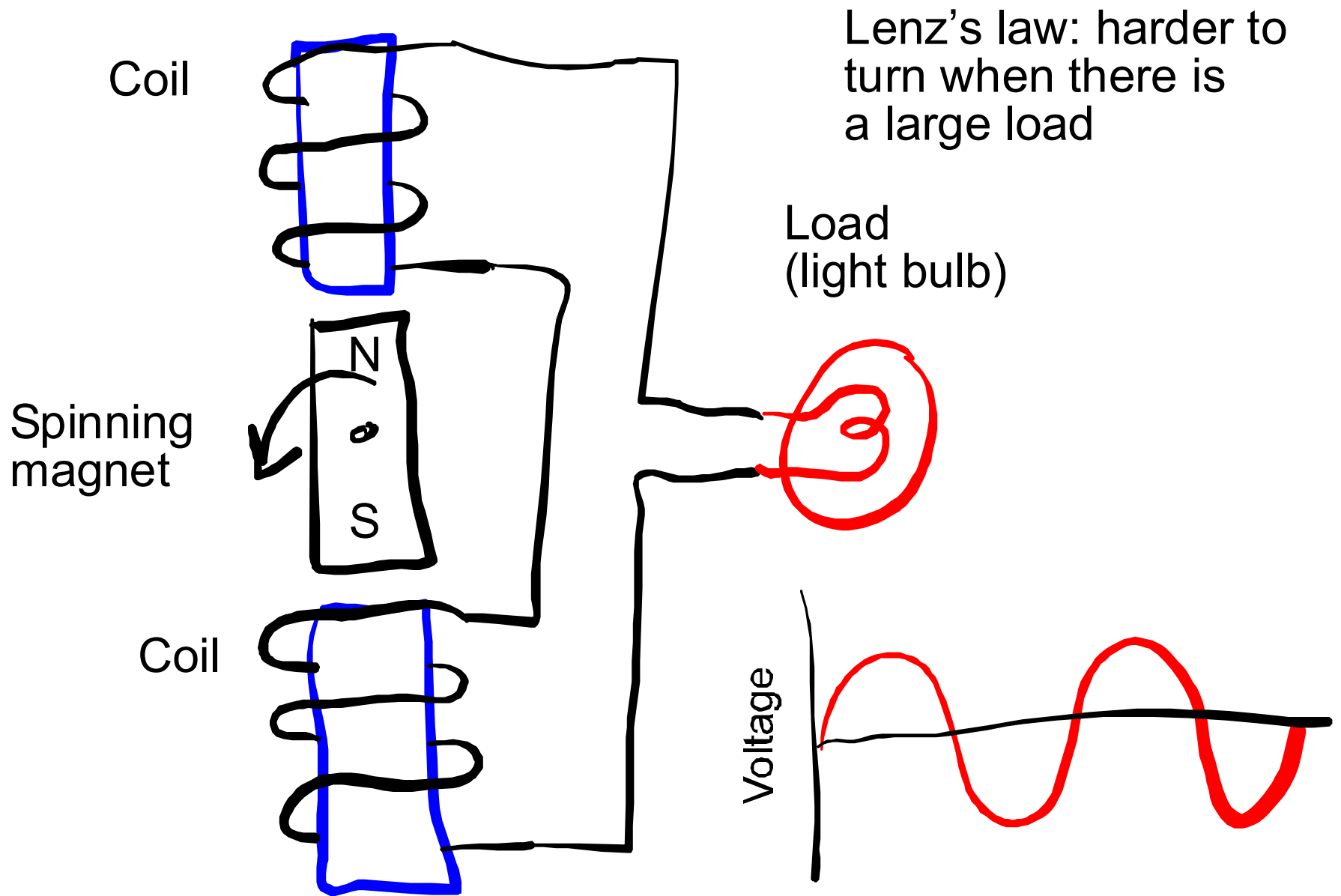


Transformer

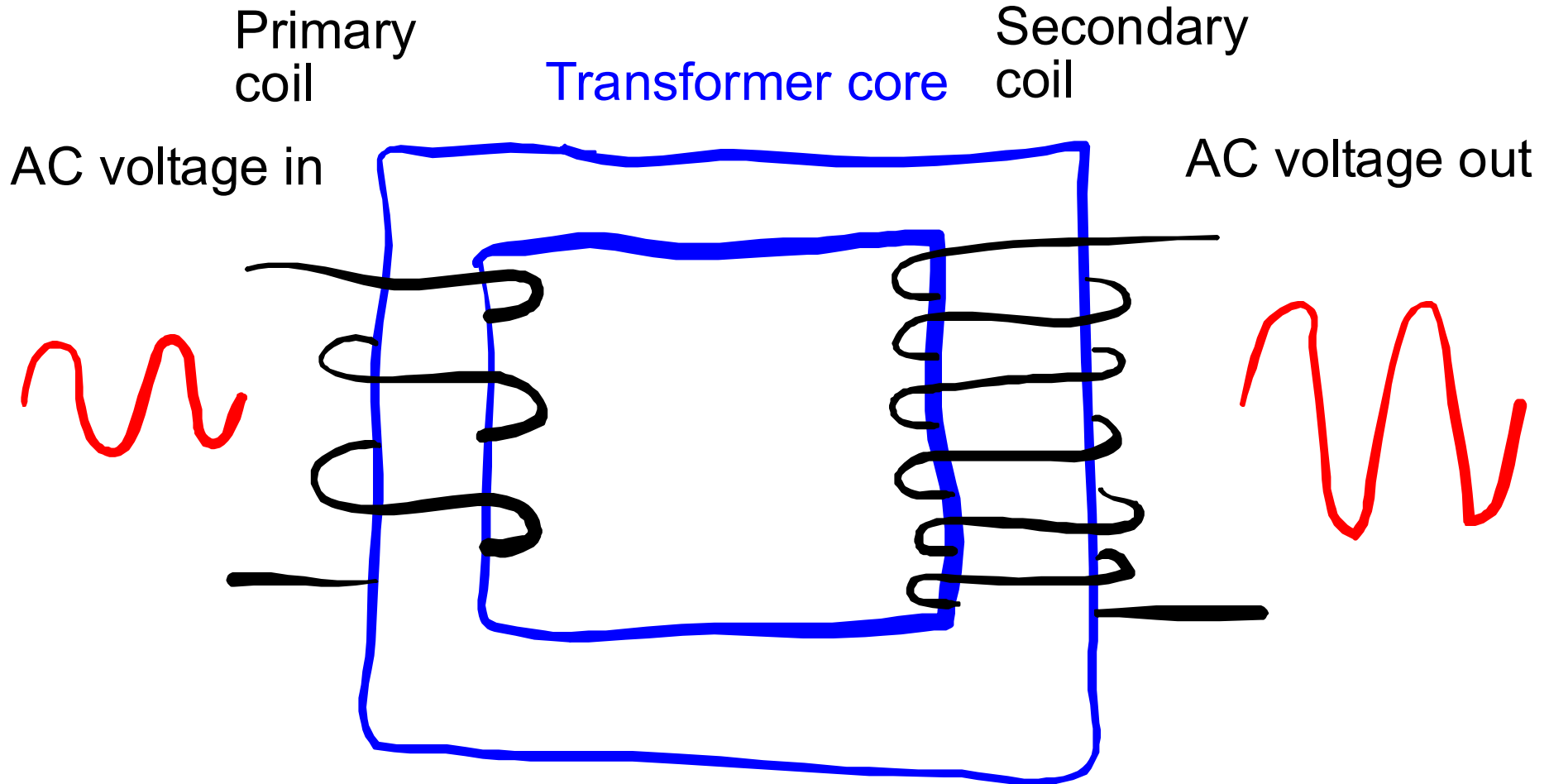

The ratio of the two voltages is the same as the ratio of the number of turns on the coils



$$V_{in} / V_{out} = \frac{\text{Number of turns in primary}}{\text{Number of turns in secondary}}$$

House Power

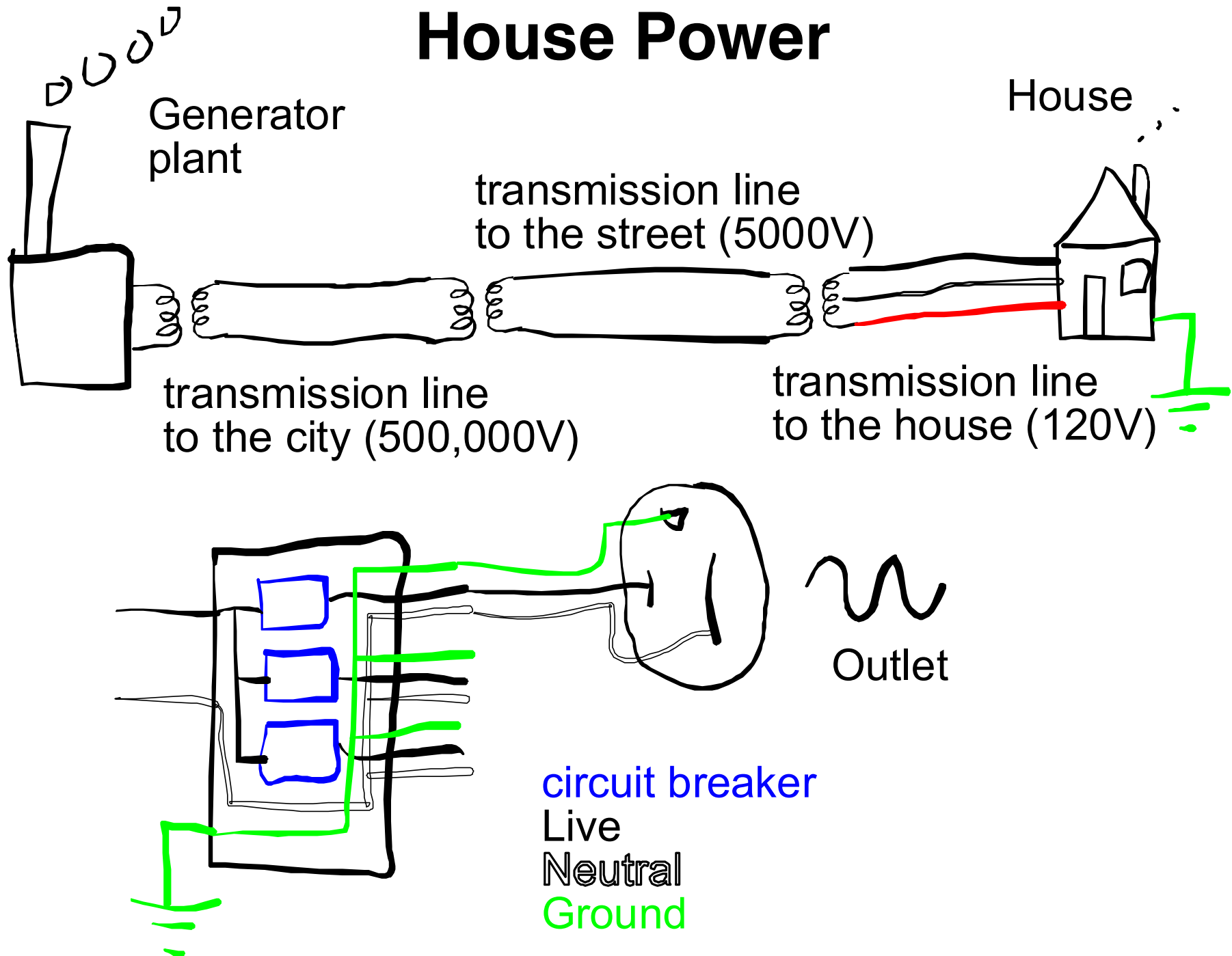

Fuses

Current

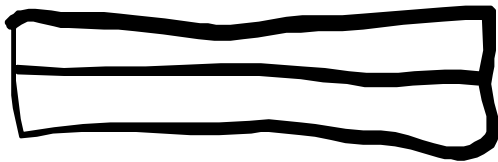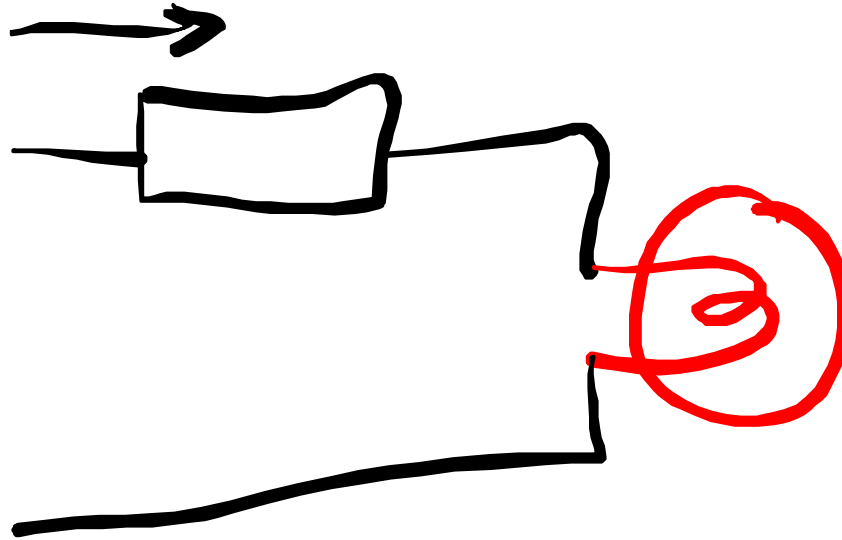


Fuse wire heats (I^2R)
eventually melts and breaks
the circuit--protects the light bulb


Circuit Breaker

bimetallic strip: two strips of metal that thermally expand at different rates

Low current

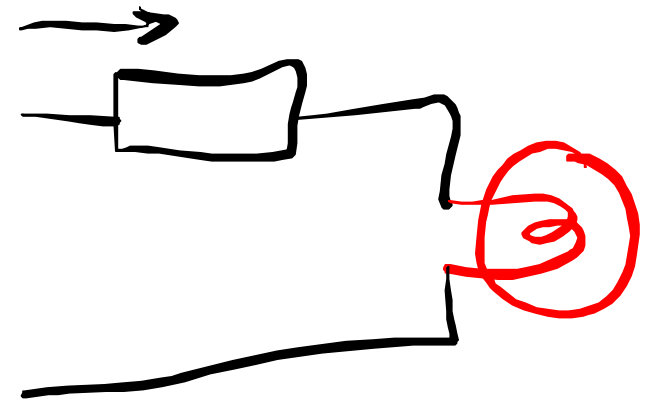


Current too high

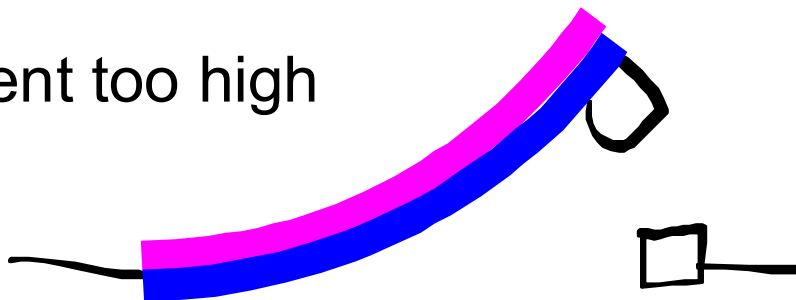

bimetallic strip heats (I^2R),
bends and pulls the contacts apart
--protects the light bulb

Ground Fault Circuit Interrupter (GFCI)

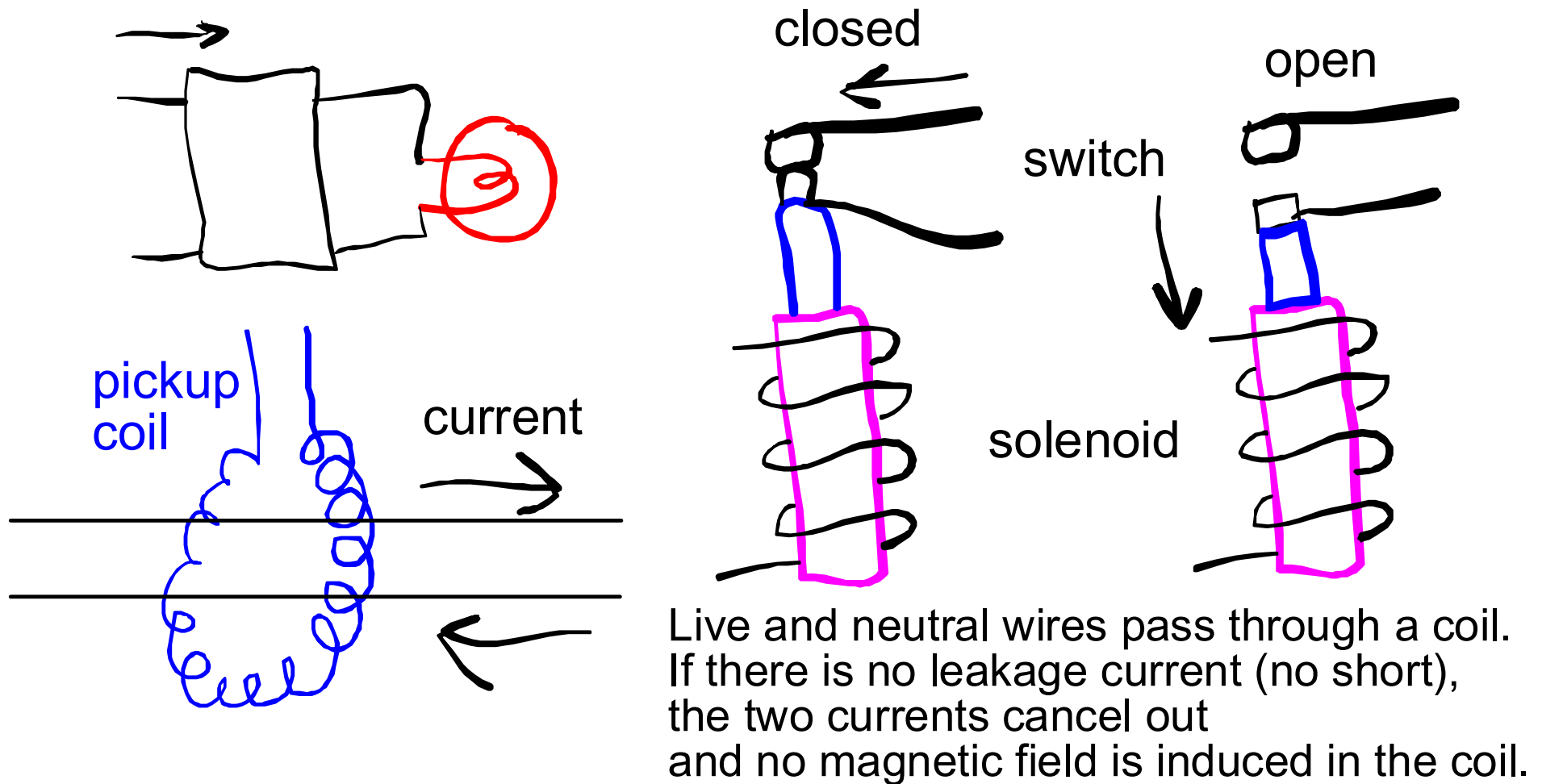

If the currents are not perfectly balanced (5mA difference), the coil will sense the difference and activate the solenoid, opening the switch and turning off the power. There are also mechanical pieces that make certain the power can not turn on again unless the reset button has been pushed.